LAB6: Design of 4-bit Ripple Carry Adder

RCA4 : a[3:0] + b[3:0]

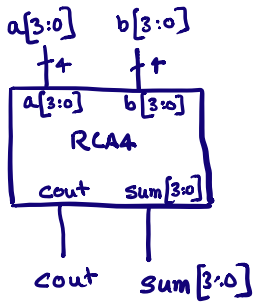

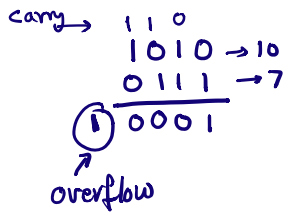

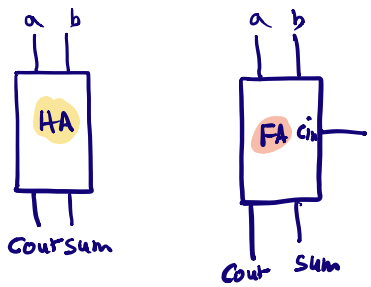

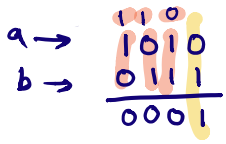

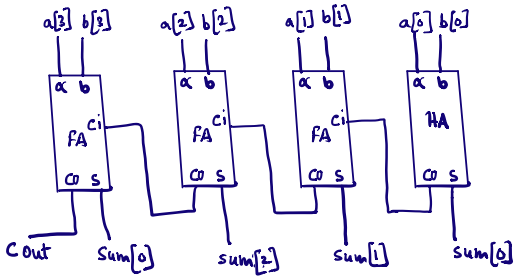

1 HA, 3 FA

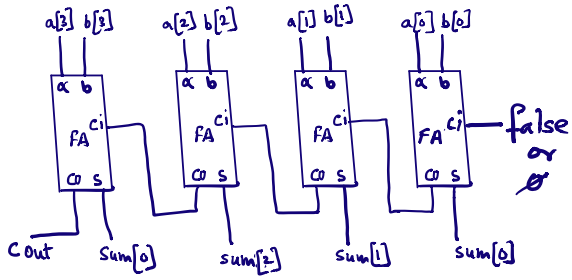

All FA's